

# IPT Summer Workshop Project Overview

2021 Summer Workshop Teams

December 2021

## 1 Introduction

In this project, the hardware and firmware required for the running of an RC car on a track using inductive power transfer (IPT) technology. The RC car used is the TAMIYA 1/10 TT-02 SUBARU IMPREZA MONTE CARLO '99 RC CAR.

## 2 Track

The track will have a length  $l$  and width  $w$  as shown in Figure 1.

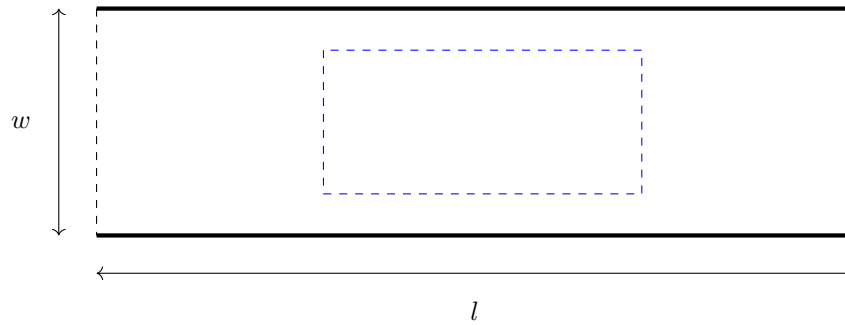


Figure 1: Simplified sketch of track top view; blue dashed rectangle represents car.

For this project, the specifications are:

- $l > 1000\text{mm}$ .
- $w = 300\text{mm}$ .
- Tolerance of car alignment:  $\pm 50\text{mm}$ .

## 3 System diagrams

Our design can be partitioned into three main sections:

1. The primary side.
2. The secondary (pick-up) side.
3. The motor driver.

### 3.1 Primary side

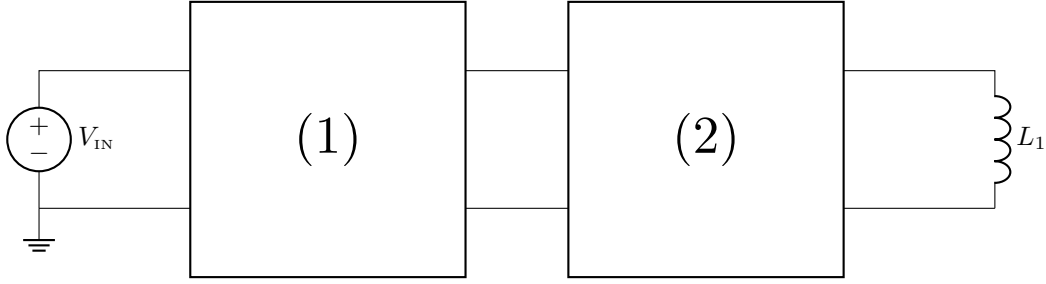


Figure 2: System diagram for the primary side

Figure 2 outlines the hardware of our primary side. A DC voltage  $30V \leq V_{IN} \leq 45V$  is used as the input. As we must have AC for IPT to work<sup>1</sup>, a **full-bridge inverter** (1) transforms the DC voltage to a high-frequency AC voltage. An **LCL** compensation network (2) with partial series compensation follows it.  $L_1$  is the primary coil.

### 3.2 Secondary side

Unlike the primary, the secondary will use **parallel** compensation via the capacitor  $C_{st}$ . A rectifier followed by a voltage regulator (1) generates a DC voltage which is stepped up to  $V_{OUT}$  via a **boost converter** (4).  $V_{OUT}$  is optimally  $10V$ <sup>2</sup> but can drop as low as  $4V$  depending on the alignment of the car with the center of the track.


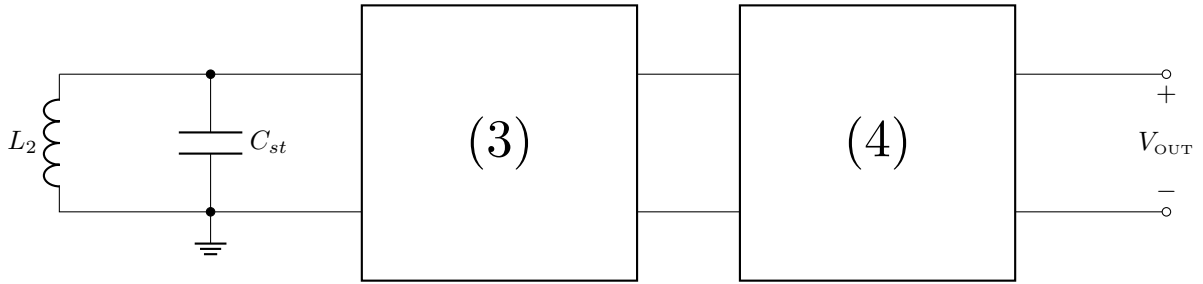


Figure 3: System diagram for the secondary side
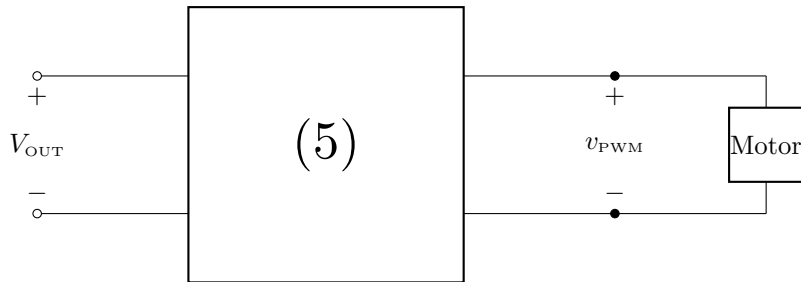
### 3.3 Motor driver

A pulse-width modulated (PWM) signal  $v_{PWM}$  used to drive the motor is produced via a full-bridge inverter (5)<sup>3</sup>. Depending on its duty cycle, the average power delivered to the motor will vary accordingly.



<sup>1</sup>As a changing current is required for a changing magnetic flux in the primary coil  $L_1$ , a DC current will not cause any changing flux and hence voltage induced in the secondary. Only AC will suffice.

<sup>2</sup>This is because the car's operating voltage is  $10V$ . It can be operated down to  $4V$  but it will have inferior performance.

<sup>3</sup>The microcontroller and hence firmware play a major role in this.